
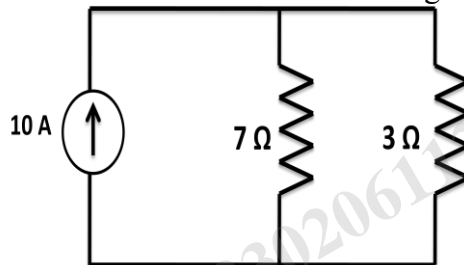


Answer any five Questions including Q No.1& 2
 Figures in the right hand margin indicates marks

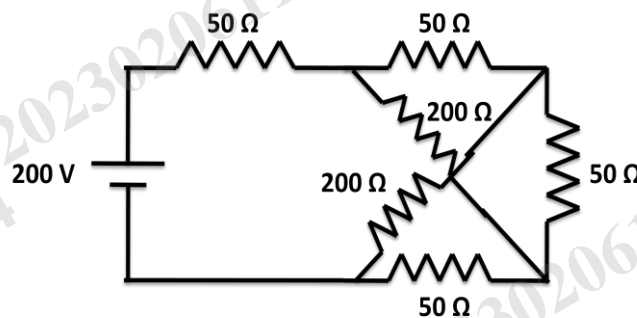
1. Answer All questions 2 x 10
- What is resonance condition?
 - State KVL and KCL.
 - Write down the difference between linear and non-linear element.
 - Define quality factor for series resonance circuit.
 - State Maximum power transfer theorem.
 - What do you mean by form factor?
 - Draw the circuit constant K high pass filter.
 - What is co-efficient of coupling?
 - Find current across 7Ω resistor in the circuit as shown in figure.




- j. Define reluctance in magnetic circuit.
2. Answer Any Six Questions 6 x 5
- Explain about different steps for solving a network by Thevenin's theorem.
 - Classify the difference between leading and lagging power factor.
 - Determine the current supplied by the battery given in the figure by KVL method.



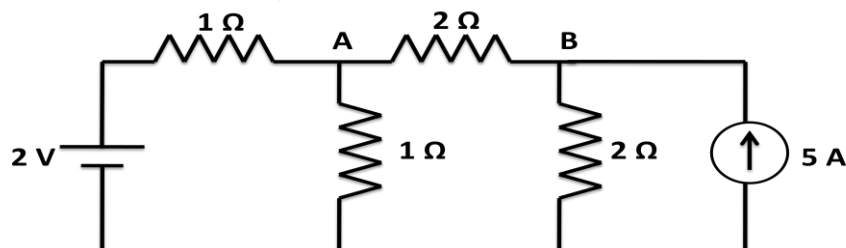
- Two impedance $Z_1 = 10 + j15\Omega$ and $Z_2 = 8 + j6\Omega$ are connected in parallel. If total current taken is 20A. Find the current taken by each branch and total power consumed by the circuit.
- Find the current across AB using nodal analysis.



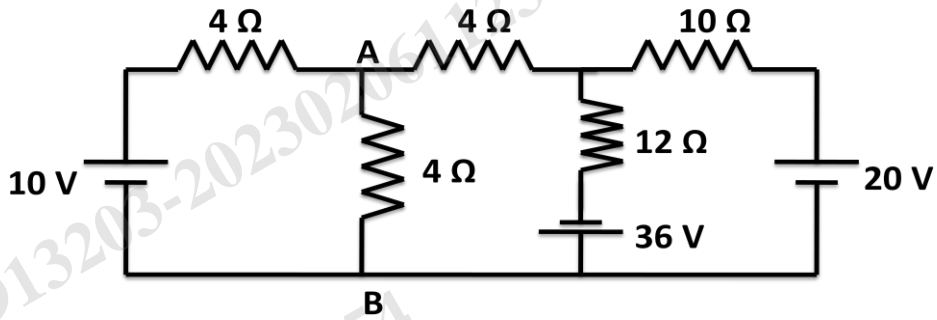
- f. Using source conversion technique reduces the following circuit to a single current source across AB.



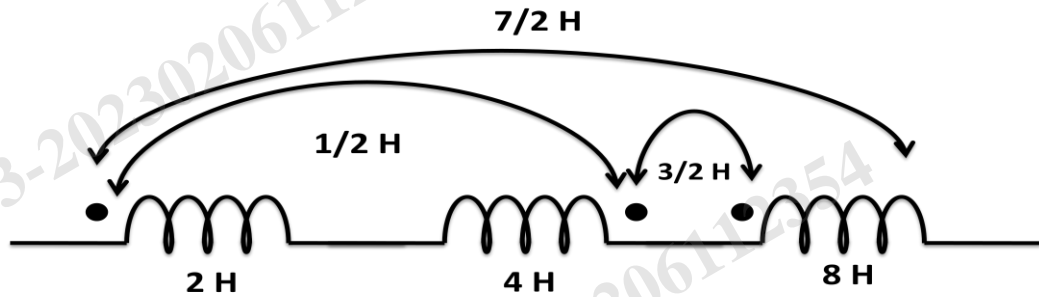- g. Find the total inductance of the three series connected coupled coil as shown in figure.



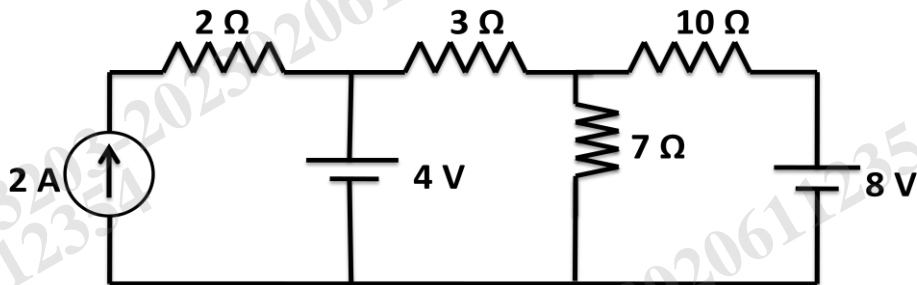3. Design a band stop, constant K filter with cut off frequencies of 5KHz to 10 KHz and nominal characteristics impedance of 300Ω . 10
4. Compare the parallel resonance circuit with a series resonance circuit. 10
5. Using superposition theorem to calculate the voltage drop across the 3 ohm resistor of figure below. All resistance value is in ohm. 10



6. Explain in detail T-Network & π -Network 10
7. Write short note on: 10
 - 1) Band pass filter
 - 2) Y-parameter