

4TH/ SEM./ ETC & COMM./E &TC/ 2023(S)

TH 4 Analog Electronics and Linear IC

Full Marks: 80

Time- 3 Hrs

Answer any five Questions including Q No.1& 2
Figures in the right hand margin indicates marks

1. Answer **All** questions 2 x 10
 - a. Draw the symbols of a) pn-junction diode and Zener diode b) pnp and npn transistor
 - b. Define Q-point.
 - c. Draw the circuit diagram of a Class-A power Amplifier.
 - d. List any two advantages of FET over BJT.
 - e. State Barkhausen criterion.
 - f. Write any two differences between amplifier and oscillator.
 - g. Draw a positive shunt clipper circuit.
 - h. Define Astable multivibrator.
 - i. Find the gain of a non-inverting op-amp having input resistance $R_{in}=100\Omega$ and feedback resistor $R_f=1000 \Omega$.
 - j. Mention any two applications of 555 timer.

2. Answer **Any Six** Questions 6 x 5
 - a. With a neat circuit diagram and appropriate waveforms, explain the working a half-wave rectifier circuit.
 - b. Define α , β and γ and establish the mathematical relationship between them
 - c. Differentiate between voltage and power amplifier. (any 5)
 - d. (i) Draw block diagram of voltage shunt feedback amplifier. [2]

(ii) Determine the voltage gain, input, and output impedance with feedback for voltage series feedback having open loop gain (A) = **150**, input resistance (R_{in}) = **1k Ω** , output resistance (R_o) = **2k Ω** for feedback fraction of β = **0.1**. [3]

- e. Draw an inverting op-amp circuit. Derive the expression for gain. If a 1V signal is given as input to it, Determine the output voltage. (Assume $R_{in}=1k\Omega$ and $R_f=10k\Omega$)
- f. Define the following parameters (along with units) of an Op-amp.
- i) Slew rate(2M)
 - ii) Input offset voltage(2M)
 - iii) Voltage gain(1M)
- g. With a neat circuit diagram, explain the working of a negative clamper circuit. Also, Draw its input and output waveforms.

- 3 Explain different types for transistor configurations and their input and output characteristics in detail. **10**
- 4 With neat sketch diagram, explain the working of Class B push pull amplifier. **10**
- 5 Classify MOSFETs and explain their input and output characteristics. **10**
- 6 Explain the operation of integrator and differentiator using OP-AMP with neat diagrams. **10**
- 7 With a neat block diagram, explain the operation of IC 555 timer. **10**