

3RD SEM /ELECTRICAL/EEE / 2020(W) OLD
EET-301 Circuit and Network Theory

Full Marks: 80


Time- 3 Hrs

Answer any five Questions including Q No.1& 2
Figures in the right hand margin indicates marks

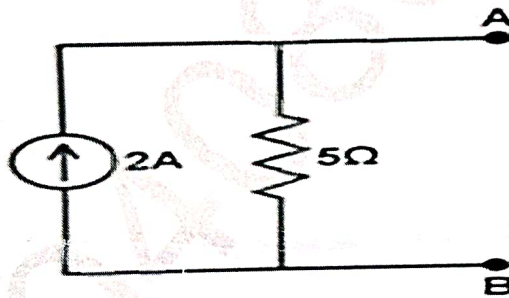1. Answer All questions

2 x 10

- State KCL and KVL?
- Define active and passive elements?
- What is reluctance?
- Define quality (Q) factor in series circuit?
- Define co-efficient of coupling?
- State Thevenin's theorem?
- What is filter in electrical circuit?
- Define mutual inductance?
- Write the units of resistance, inductance, capacitance and impedance?
-




Convert the current source into voltage source?

2. Answer Any Six Questions

6 x 5

- Explain B-H curve in magnetic circuit?
- State and Explain maximum power transfer theorem?
- What is power factor? Draw power triangle.
- Give a classification of filters?
- A series RLC circuit containing a resistance of 12Ω , an inductance of 0.15H and a capacitor of $100\mu\text{F}$ are connected in series across a 100V , 50Hz supply. Calculate the total circuit impedance, circuit current?

f.

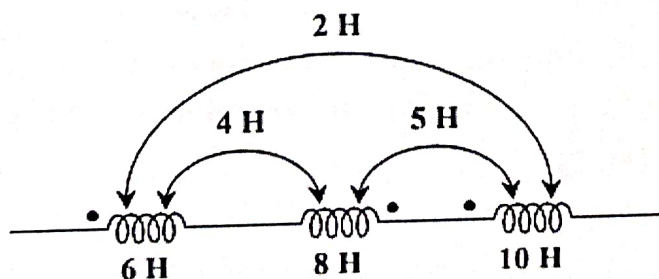


For the three coupled coil, calculate the total inductance?

g Derive the relation between line and phase quantity in star connection?

3 Design a K-type band-pass filter having a design impedance of 500ohm and cut-off frequencies 1 KHZ and 10KHZ? 10

4 10

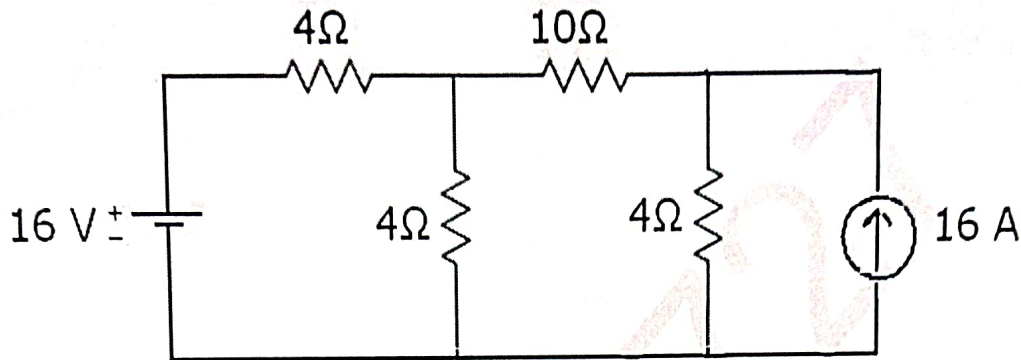


Using Super-position principle find the current in 10 ohm resistor?

5 (a)What is resonance condition? Derive the expression for resonant frequency in RLC series circuit? 5

(b)State and explain Milliman's Theorem? 5

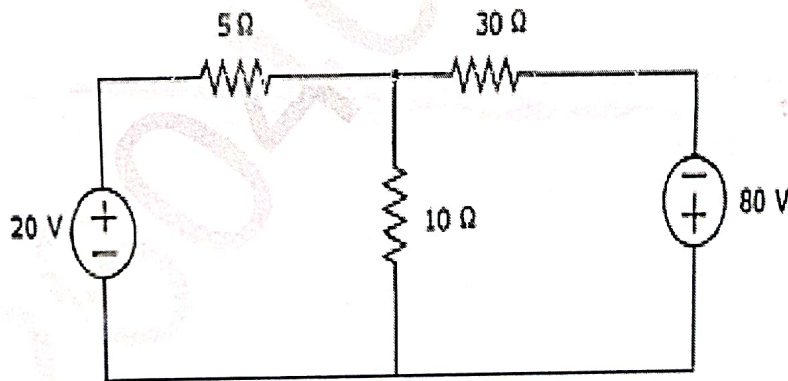6 (a)Using mesh analysis find the current in 10 ohm resistor? 10



(b)Find the analogy between Electric and magnetic circuit?

7 Write short note on any two 5*2=10

(a)Open circuit (Z) parameter

(b)Steady state and Transient response

(c)resonant frequency for a tank circuit

*A sem
10/1/2021*

3RD SEM./ELECT/E&M/EEE/EE(I&C)/ELECT[PT]/2020(W)NEW
TH2-CIRCUIT AND NETWORK THEORY

Full Marks: 80

Time: 3 Hours

Answer any Five Questions including Q No. 1 & 2
Figures in the right hand margin indicates marks

1. Answer all the questions


10x2

- What is reactive power? State its SI unit
- What do you mean by nodal analysis of AC networks?.
- State the superposition theorem.
- Define (i) Bandwidth (ii) Q factor in series circuit
- What is power factor and power triangle?
- Give an example of (i) Active Element (ii) Linear Element
- What do you mean by coefficient of coupling in coupled circuits?
- Define (i) Reluctance (ii) Permeance
- Classify the filters on the basis of frequency characteristics.
- What are short-circuit admittance parameters?

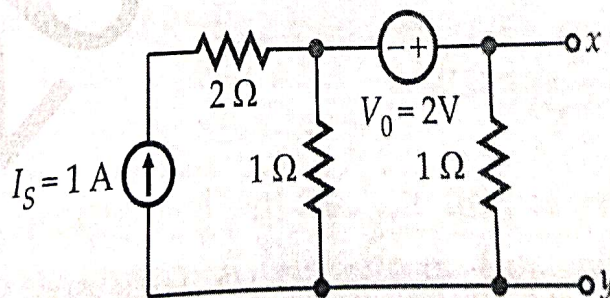2. Answer any six questions


6x5

- Write down the analogies between electric and magnetic circuits.
- Find the Thevenin's equivalent to the left of terminals x-y in the below network.



- How the 3 phase power is measured by two wattmeter method?
- Write a short note on hybrid (h) parameters.
- Explain the sinusoidal response of parallel R-C circuit
- Describe briefly about π section of a circuit network

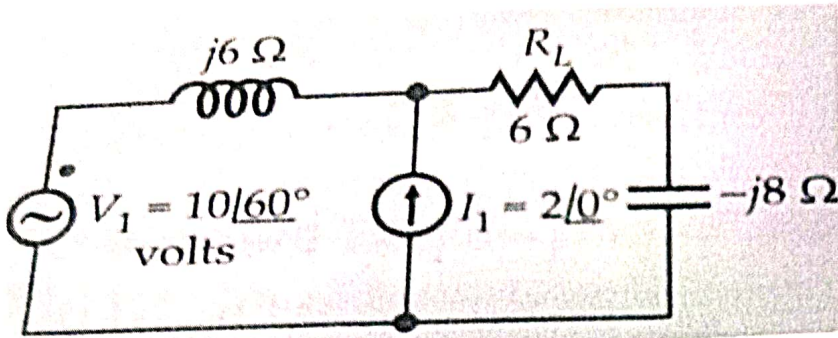g) Find the current in the resistor (R_L) using the principle of superposition theorem in below network.



- | | | |
|----|---|----|
| 3. | Derive the relation between phase and line quantities in star connection. | 10 |
| 4. | Describe about the resonant frequency of series resonance and parallel resonance circuit. | 10 |
| 5. | Explain the transient response of series R-L circuit having DC Excitation. | 10 |
| 6. | Write short notes on (i) Constant K low pass filter (ii) Constant K Band pass filter. | 10 |
| 7. | Write short notes on (i) Hysteresis Loop (ii) Source Transformation technique. | 10 |

3RD SEM./ELE & MECH./ EEE/ ELE./ EE(I & C)/ 2023(W)NEW


Th-2 Circuit & Network Theory

Full Marks: 80


Time- 3 Hrs

Answer any five Questions including Q No.1& 2
Figures in the right hand margin indicates marks

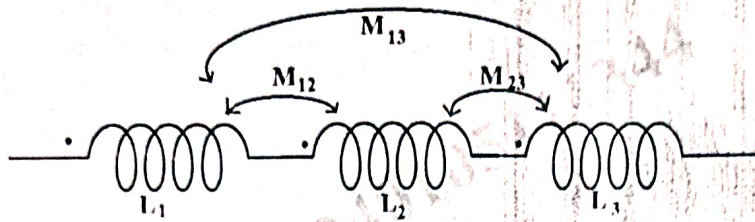1. Answer All questions 2 x 10
 - a. What are bilateral and unilateral elements and give some examples.
 - b. State KCL and KVL.
 - c. State Thevenin's theorem.
 - d. State different powers and draw the power triangle.
 - e. State the condition for maximum power to be transferred in the circuit. Write down the expression of maximum power.
 - f. Define quality factor.
 - g. Define coefficient of coupling.
 - h. Write down the condition for series resonance and the expression of frequency.
 - i. State the open circuit parameters of a two port network.
 - j. Define filter. Write down the types of filters
2. Answer Any Six Questions 6 x 5
 - a. Explain B-H curve briefly with a neat diagram.
 - b. Give a comparison between magnetic circuit and Electric circuit.
 - c. Find the total inductance of the three series connected coupled coils as shown in the figure. Given: $L_1 = 1 H, L_2 = 2 H, L_3 = 5 H, M_{12} = 0.5 H, M_{23} = 1 H, M_{13} = 1 H$.



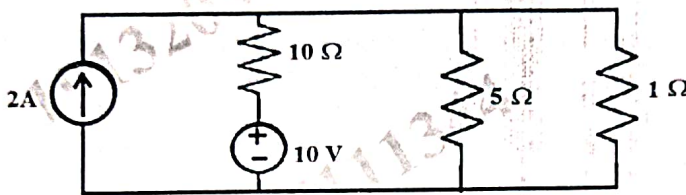
d. Find the power loss in 1 ohm resistor by Thevenin's theorem.




e. What are the properties of resonance?

f. A coil having resistance of 10 ohm and inductance of 1H is switched on to a direct voltage of 100 volt. Calculate the rate of change of the current (a) at the instant of closing the switch (b) when $t = L/R$.


g. Find the value of I_1

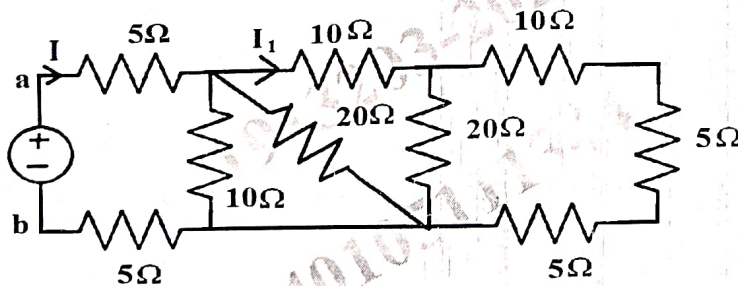

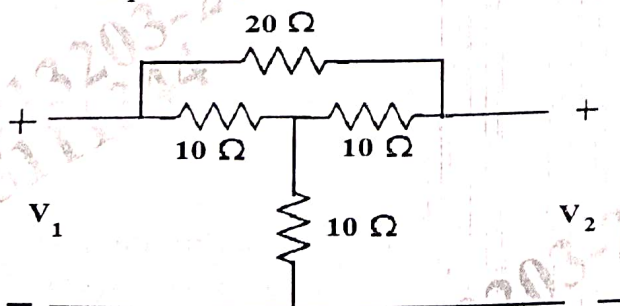3. Find the Z-parameters of the circuit as shown in the figure.




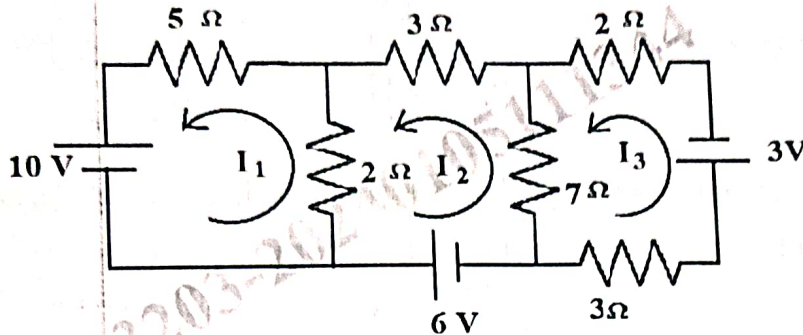4. Find I_1, I_2 and I_3 by using Mesh analysis.



5 Derive the relation between phase and line quantities in star and Delta Connection of a 3-phase circuit. 10

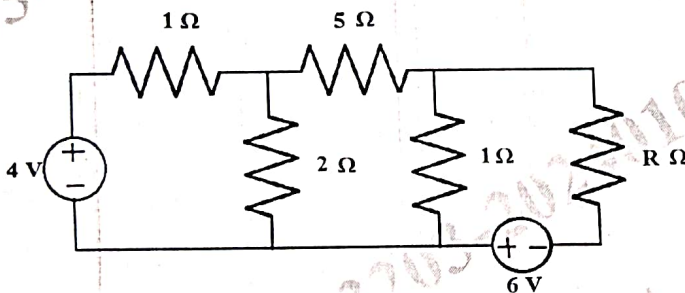6 Find the value of 'R' in the circuit of figure as shown below such that maximum power transfer takes place. What is the amount of this power? 10



7 Design a constant k-low pass filter(both Π and T) having $f_c = 2\text{KHz}$ and design impedance $R_0 = 600\Omega$. Obtain the value of attenuation at 4 kHz. 10

3RD SEM./ELE. & MECH./EEE./ELE./EE(INST. & CONT.)/ 2024(W)

TH2 Circuit & Network Theory

Full Marks: 80


Time- 3 Hrs

Answer any five Questions including Q No.1& 2
 Figures in the right hand margin indicates marks

1. Answer All questions

2 x 10

a.

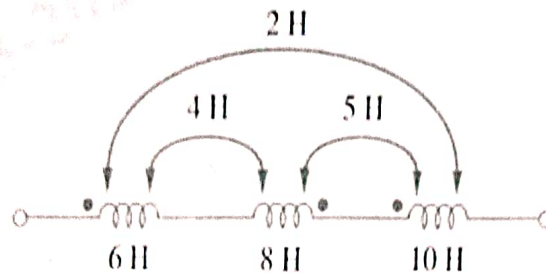


Find the total inductance of the three series connected coupled circuit.

- b. A current of 15 A divides between two branches in parallel resistance of 8 ohm & 16 ohm respectively. Calculate the current in each branch.
- c. What is passive element? Give two Examples.
- d. What are self-inductance and mutual inductance?
- e. What is the true power consumed in a 30V series RLC circuit if $Z = 20$ ohm and $R = 10$ ohm?
- f. State Q-factor for series resonant circuit.
- g. Write the analogy between the Electric and Magnetic circuits.
- h. Define time-constant in R-C circuit.
- i. What do you mean by Transmission parameters?
- j. If the voltage in an ac circuit is represented by the equation, $v = 220\sqrt{2} \sin(314t - \phi)$ Volt . Calculate (i) peak value of the voltage (ii) rms value of the voltage


2. Answer Any Six Questions

5 x 6

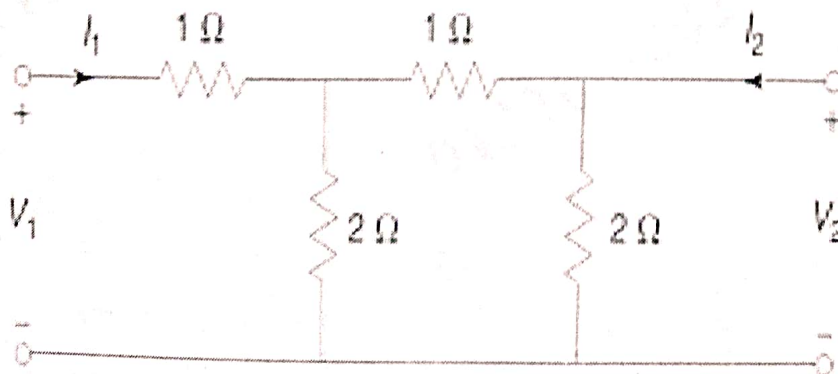- a. A series RLC circuit has $R=10\Omega$, $L=0.5H$ and $C=40\mu F$. The applied voltage is 100V. Find, (a) Resonant frequency (b) Quality factor of a coil (c) Bandwidth (d) Upper and lower Half power frequencies. 1+1+1+2
- b. Design K-Type Band Pass Filter having a design impedance Of 500 Ohm and Cut-Off Frequencies 1Khz and 10Khz.
- c. Find Z parameter for the network given below



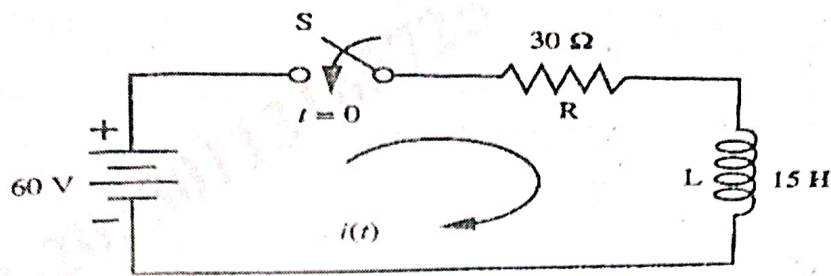- d. Derive the expression for the current in the below circuit when the switch, S is closed at $t=0$.




- e. State Maximum Power Transfer theorem. Derive the condition of maximum power transfer.
- f. Find the number of turns required to produce a flux density of 2T in a core of mean magnetic length of 260cm when the coil carries a current of 5A. Assume the permeability of the core is 1000.
- g. Derive the expression for Delta connected resistances in terms of Star connected resistances.


Answer **Any Three** Questions

3. Use super mesh analysis method, determine all mesh currents.

10

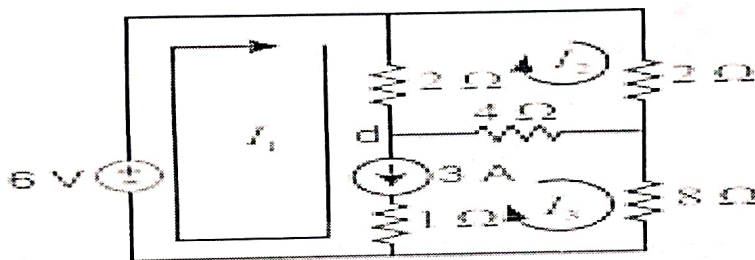

4.

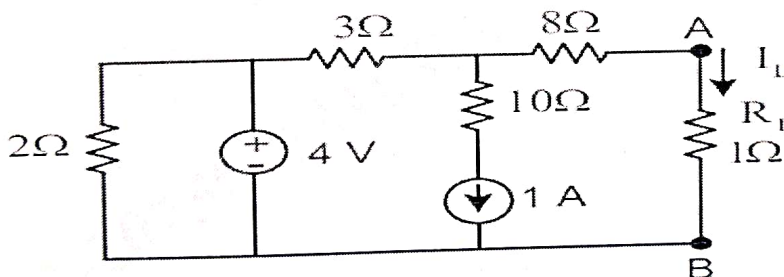

10

Determine the current through the load resistance 1 ohm using Norton's theorem.

5. Derive the expression of 3-phase power and power factor by using 2-wattmeter method. 10
6. Explain hysteresis loop with diagram. 10
7. Two impedance $Z_1 = (8 + j6)$ and $Z_2 = (3 - j4)$ are in parallel. If the total current of the combination is 25A, find the current taken and power consumed by each impedance. 10