

Th. 2 - CIRCUIT & NETWORK THEORY

Full Marks: 80

Time : 3 Hours

Answer any FIVE Questions including Q No. 1 & 2

Figures in the right hand margin indicates marks

1. Answer ALL the Questions:
  - (a) Define Retentivity ?
  - (b) What do you mean by Coefficient of Coupling ?
  - (c) Draw the power triangle and derive the formula for apparent power?
  - (d) State Superposition Theorem.
  - (e) What is Bilateral element ? Give at least two examples?
  - (f) Define Quality Factor.
  - (g) Define Filter in electrical circuit
  - (h) What is power factor?
  - (i) State Blondel's Theorem.
  - (j) Find the current across  $5\Omega$  resistor in the circuit as shown in Figure 1.

[2x10]

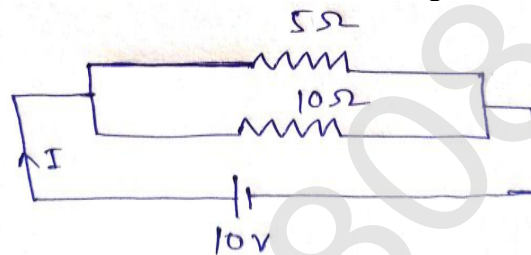


Figure 1

2. Answer any SIX questions:
  - (a) Explain Briefly the 3ph power measurement by 2-Wattmeter method for Star connection load only?
  - (b) Find the total inductance of the three series connected coupled coil as shown in the Figure 2.

[5x6]

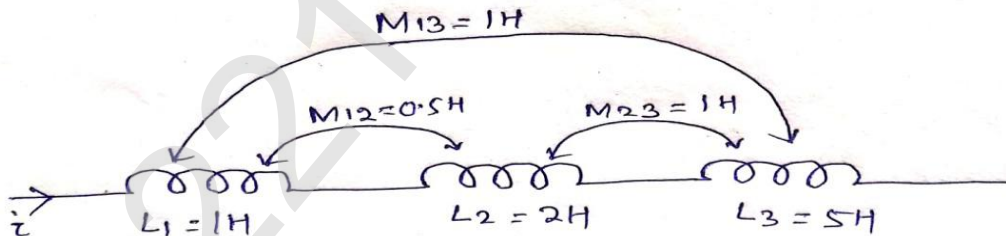


Figure 2

- (c) State and Explain Maximum Power Transfer Theorem.
- (d) Find the current in series R-L circuit having  $R = 2\Omega$  AND  $L = 10\text{ H}$  while D.C voltage of 100V is applied. What is the value of this current after 5sec of switching on ?
- (e) Derive the Relation between Line and Phase quantities in STAR connection?
- (f) In series RLC circuit has  $R = 2\Omega$ ,  $L = 2\text{mH}$  and  $C = 10\mu\text{F}$ . Calculate (i) Q- Factor of the circuit (ii) Bandwidth (iii) The Resonant frequency (iv) the half power frequency  $f_1$  and  $f_2$ .
- (g) The unbalanced Bridge circuit is shown in Figure 3. Find the value of current in  $R_L = 50\Omega$

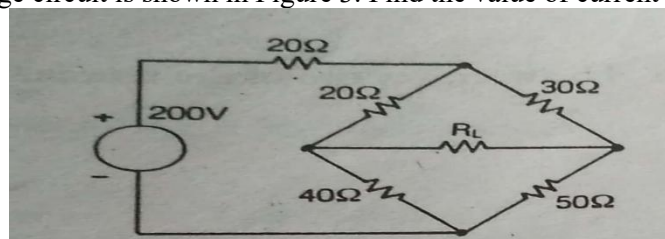


Figure 3

3. Consider the Figure 4 as shown below. Find the voltage at different node by using SUPERNODE analysis? [10]

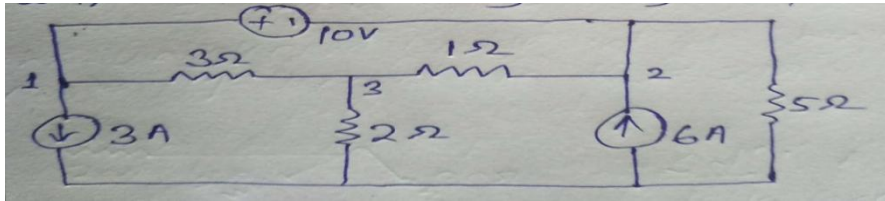


Figure 4

4. Explain Briefly Hysteresis loop in a ferromagnetic material? [10]
5. Obtain the open circuit parameter (Z- Parameter) and loop quantities of the network shown in Figure 5. [10]

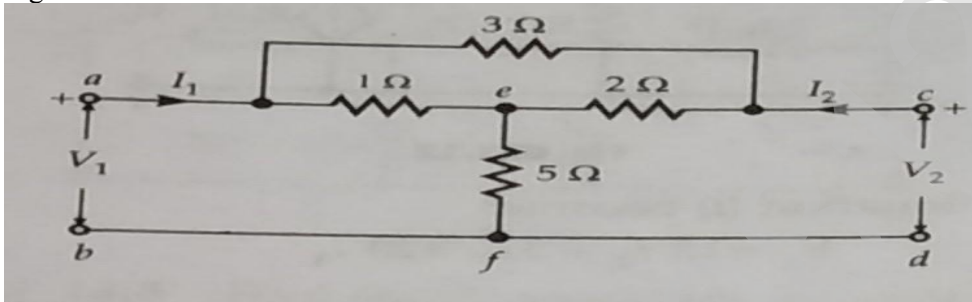


Figure 5

6. Find the current in the 3Ω resistor for the circuit as shown in Figure 6 by using Thevinin Theorem. [10]

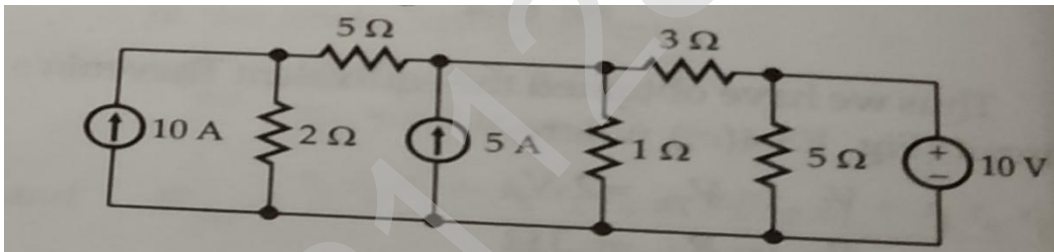


Figure 6

7. Design a Prototype Band Pass Filter to match with a load of 600Ω and allow frequencies between 3KHZ and 6KHZ. [10]